



Introduction to Digital Signal Processing on FPGA

Qiang Du

USPAS Houston, January 25, 2023

Lawrence Berkeley National Lab

Table of contents


1. Introduction to digital circuit design
2. Programmable Logic Cells
3. Routing
4. Clocks
5. Putting things together

Introduction to digital circuit design

FPGA: Field Programmable Gate Array

Typical elements:

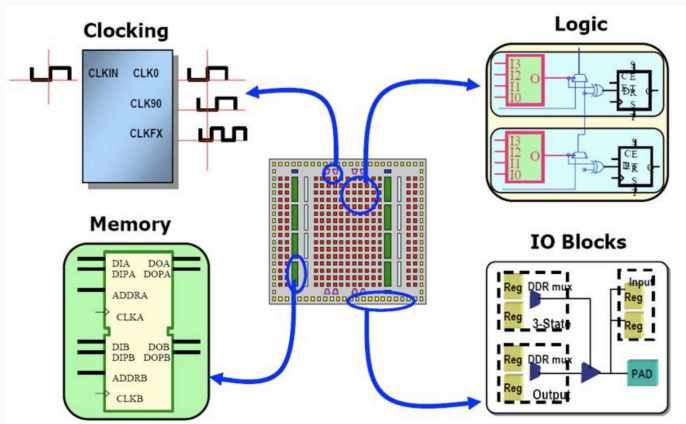- Random Access Memory (RAM)
- Logic gates
- DSP
- Input / Outputs
- Clock management units
- Phase Locked Loop (PLL)
- Multi-Gigabit Transceivers
- ...



How to design a digital circuit


Schematic Circuit Design

- Advantage
 - Block diagrams, imply physical hardware
 - Intuitive, match gate-level logic
- Disadvantage
 - Requires graphical editor tool
 - Hard to track changes
 - Scalability suffers when hierarchy grows

Hardware Description language (HDL)

- Advantage
 - Text based, no special tool needed
 - Version control friendly
 - Scalable (similar to Object Oriented Programming)
- Disadvantage
 - Not so intuitive
 - Not directly showing the hardware primitives

Digital circuit design methodology

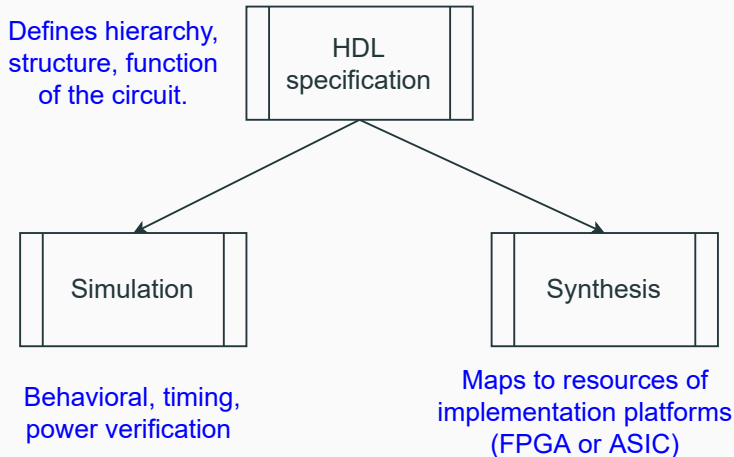

Lab 3: LED blinker, Lab 4: Frequency counter

Hardware Description Languages

	Strong typing	Style	typedef	Structures	Class	Interface
VHDL	Yes	ADA	Yes	Yes	No	Partial
Verilog	No	C	No	No	No	No
SystemVerilog	Partial	C	Yes	Yes	Yes	Yes

VHDL More syntactic overhead, semantically close to Verilog

Verilog Mature set of commercial / open-source tools

SystemVerilog Enhancement to Verilog, less-mature tools


Verilog modules and instantiation: combinational and sequential logic

'led_test.v'

```
module led_test #(                                // module define
    parameter MSB = 27 )(                        // parameter define
    input  clk ,
    input  reset ,                               // port define
    output [3:0] led ) ;                         // multi-bit signal
reg [31:0] cnt=0;                               // register that holds states
always @(posedge clk) begin                    // sensitivity list , non-blocking
    cnt <= reset ? 32'h0 : cnt + 1'b1;         // constant , mux,
end                                              // assignment (defer), sequential
assign led = cnt[MSB:MSB-3];                   // blocking assignment (no defer)
endmodule                                       // combinational
```

Use Non-blocking for sequential logic. Use blocking for combinatorial logic. details

D Flip-flop (FF)

 


Xilinx Primitive: D Flip-Flop with Clock Enable and Synchronous Reset, FDRE

Verilog example

```
module dff(  
    input D,  
    input clk ,  
    input reset ,  
    output reg Q  
);  
    always @(posedge clk) begin  
        if (reset) // synchronous reset  
            Q <= 1'b0;  
        else  
            Q <= D;  
    end  
endmodule
```

Look-up Table (LUT)

 

Xilinx Primitive: 4-Bit Look-Up Table, LUT4

Verilog example: Combinational Logic

```
module lut4 (  
    input [3:0] I,  
    output O  
);  
    assign O = I[0] | (&I[3:1]);  
endmodule
```


Internal Random Access Ram (RAM)

- First In, First Out buffer (FIFO)
- Single, Dual, Multiple port Memory
- 1:N or N:1 aspect ratio
- Clock domain crossing

Verilog example: Dual port RAM

```
module dpram #(
    parameter AW = 8,
    parameter DW = 8
) (
    input  clka, clkb, wena,
    input  [AW-1:0] addra, addrb,
    input  [DW-1:0] dina,
    output [DW-1:0] douta, doutb
);
    parameter SIZE = (32'b1<<AW)-1;
    reg  [DW-1:0] mem[SIZE:0];
    reg  [AW-1:0] ala=0, alb=0;

    assign douta = mem[ala];
    assign doutb = mem[alb];
    always @(posedge clka) begin
        ala <= addra;
        if (wena) mem[addra]<=dina;
    end
    always @(posedge clkb) begin
        alb <= addrb;
    end
end
endmodule
```

How to do 4-bit adding using logic gates?

Do it by hand:

	a3	a2	a1	a0
+	b3	b2	b1	b0
c	r3	r2	r1	r0

Add a0 and b0:

a0	b0	r0	c0
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$r = a \oplus b, \quad c = a \& b$$


Add a1 and b1:

c0	a1	b1	r1	c1
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


$$r = a \oplus b \oplus c, \quad c_o = a \& b + a \& c_i + b \& c_i$$

Programmable Logic Cells

Logic Cell

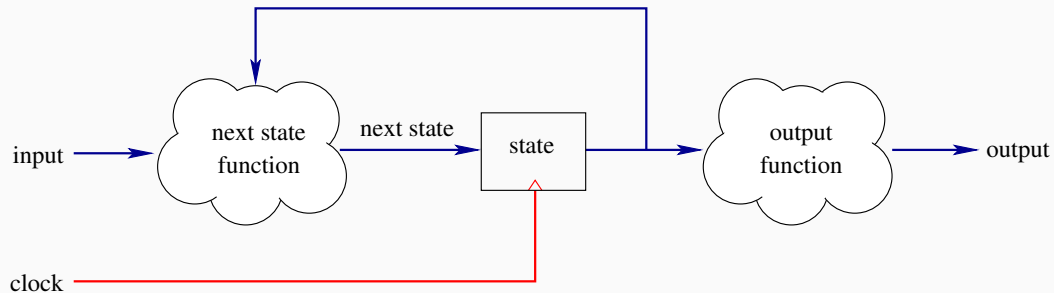


Logic Cell: Simplist concept

 


And, or, xor, multiplex, two-way mux with force-to-constant

 Logic Cell: Simplist concept with a carry chain




Add, subtract, gated-add, add/sub

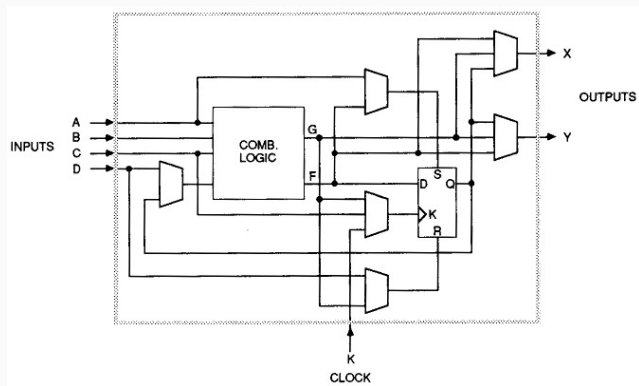
History: First commercial FPGA (XC2064) in 1985 had 64 of these cells



 History: Modern carry chain (XC4000) from 1991



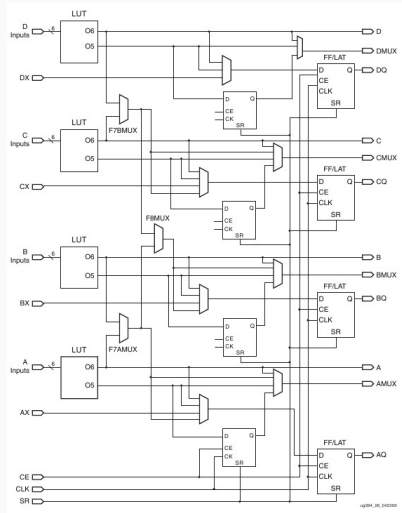History: Modern carry chain (Spartan6) from 2009



Datasheet: Xilinx 7 series family, September 2020

Table 1: 7 Series Families Comparison

Max. Capability	Spartan-7	Artix-7	Kintex-7	Virtex-7
Logic Cells	102K	215K	478K	1,955K
Block RAM ⁽¹⁾	4.2 Mb	13 Mb	34 Mb	68 Mb
DSP Slices	160	740	1,920	3,600
DSP Performance ⁽²⁾	176 GMAC/s	929 GMAC/s	2,845 GMAC/s	5,335 GMAC/s
MicroBlaze CPU ⁽³⁾	260 DMIPs	303 DMIPs	438 DMIPs	441 DMIPs
Transceivers	–	16	32	96
Transceiver Speed	–	6.6 Gb/s	12.5 Gb/s	28.05 Gb/s
Serial Bandwidth	–	211 Gb/s	800 Gb/s	2,784 Gb/s
PCIe Interface	–	x4 Gen2	x8 Gen2	x8 Gen3
Memory Interface	800 Mb/s	1,066 Mb/s	1,866 Mb/s	1,866 Mb/s
I/O Pins	400	500	500	1,200
I/O Voltage	1.2V–3.3V	1.2V–3.3V	1.2V–3.3V	1.2V–3.3V
Package Options	Low-Cost, Wire-Bond	Low-Cost, Wire-Bond, Bare-Die Flip-Chip	Bare-Die Flip-Chip and High- Performance Flip-Chip	Highest Performance Flip-Chip

Notes:

1. Additional memory available in the form of distributed RAM.
2. Peak DSP performance numbers are based on symmetrical filter implementation.
3. Peak MicroBlaze CPU performance numbers based on microcontroller preset.

© Copyright 2010–2020 Xilinx, Inc. Xilinx, the Xilinx logo, Alveo, Artix, Kintex, Spartan, UltraScale, Versal, Virtex, Vivado, Zynq, and other designated brands included herein are trademarks of Xilinx in the United States and other countries. PCI, PCI Express, PCIe, and PCI-X are trademarks of PCI-SIG. All other trademarks are the property of their respective owners.

Datasheet: Xilinx Ultrascale series family, December 2022

Table 1: Device Resources

	Artix UltraScale+ FPGA	Kintex UltraScale FPGA	Kintex UltraScale+ FPGA	Virtex UltraScale FPGA	Virtex UltraScale+ FPGA	Zynq UltraScale+ MPSoC	Zynq UltraScale+ RFSoc
MPSoC Processing System						✓	✓
RF-ADC/DAC							✓
SD-FEC							✓
System Logic Cells (K)	82–308	318–1,451	356–1,843	783–5,541	862–8,938	81–1,143	489–930
Block Memory (Mb)	3.5–10.5	12.7–75.9	12.7–60.8	44.3–132.9	23.6–94.5	3.8–34.6	22.8–38.0
UltraRAM (Mb)			0–81		90–360	0–36	13.5–45.0
HBM DRAM (GB)					0–16		
DSP (Slices)	216–1,200	768–5,520	1,368–3,528	600–2,880	1,320–12,288	216–3,528	1,872–4,272
DSP Performance (GMAC/s)	1,860	8,180	6,287	4,268	21,897	6,287	7,613
Transceivers	4–12	12–64	16–76	36–120	32–128	0–72	8–16
Max. Transceiver Speed (Gb/s)	16.3	16.3	32.75	30.5	58.0	32.75	32.75
Max. Serial BW (bidir) (Gb/s)	393	2,086	3,268	5,616	8,384	3,268	1,048
Memory Interface Perf (Mb/s)	2,400	2,400	2,666	2,400	2,666	2,666	2,666
I/O Pins	128–304	312–832	280–668	338–1,456	208–2,072	82–668	152–408

Xilinx is creating an environment where employees, customers, and partners feel welcome and included. To that end, we're removing noninclusive language from our products and related collateral. We've launched an internal initiative to remove language that could exclude people or reinforce historical biases, including terms embedded in our software and IPs. You may still find examples of non-inclusive language in our older products as we work to make these changes and align with evolving industry standards. Follow this [link](#) for more information.

DS890 (v4.3) November 7, 2022

www.xilinx.com

Product Specification


1

Routing


Routing

Well documented routing from 1998 (XC3000).

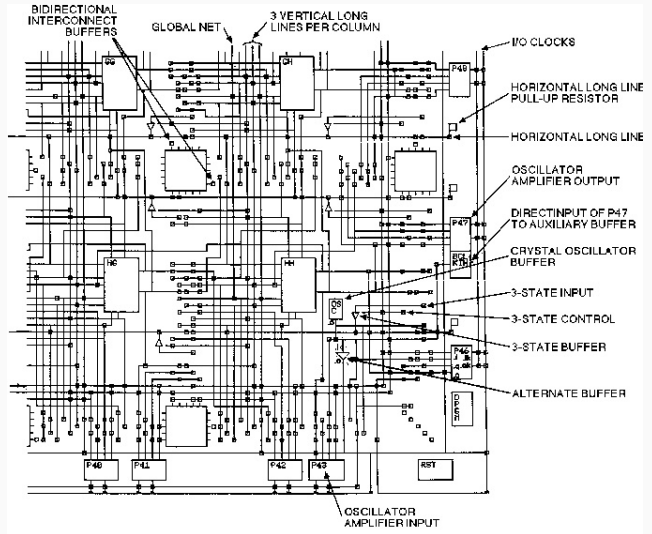
Routing needs scale super-linearly with chip size; routing hardware is now much more capable, complex, and less well documented.



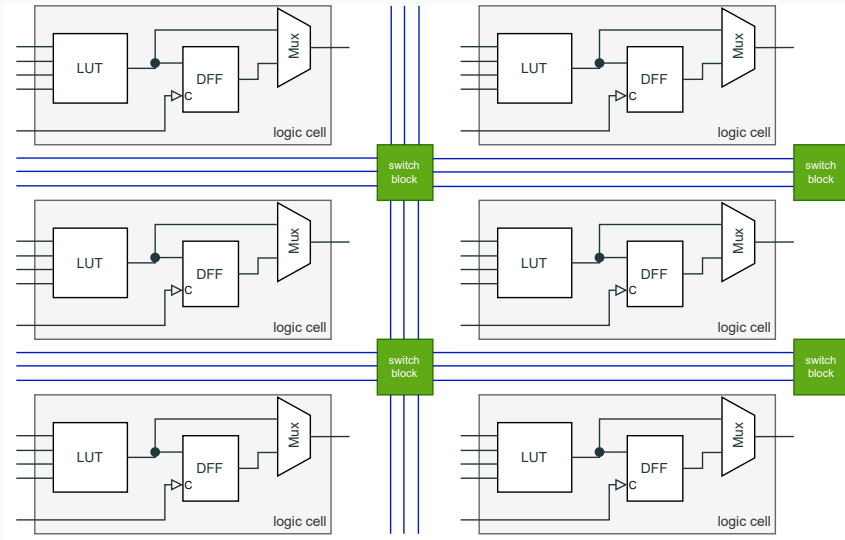Programmable Logic: Interconnect Logic Cells



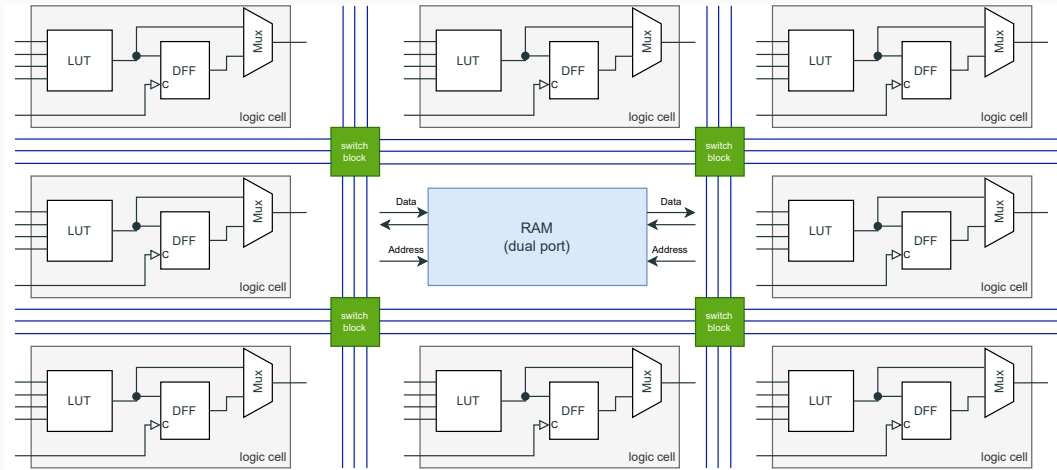Programmable Logic: Interconnect Logic Cells with RAM



Clocks

- Handful of well-defined domains: good
- Clock-enable on registers: good
- Low latency data path involving multiple clock domains: bad
- Gated clocks: terrible

As FPGAs get larger and faster, demands on the clock tree get harsher. Newer chips deprecate global clocks; clock-domain crossing is needed between zones. Think of it as several chips in one package (sometimes literally true). Tools and design practices must be adjusted to cope.

Generally our designs have at least two clock domains:

- High throughput DSP has no wiggle-room on its speed, has to match ADC
- Communications (e.g., Ethernet, USB, VME, PCI)

Many unavoidable reasons to increase from the minimum, e.g., White Rabbit leaf node needs one or two more domains to function correctly.

If you have lower throughput DSP stuff to do, *and* wish to re-use someone else's "IP" (e.g., a soft core) that may not make timing with your main DSP clock, you may need to generate a subharmonic clock for that sub-circuit. That will count as a new clock domain! Example:


- Z80 from OpenCores at 40 MHz
- LM32 at 80 MHz

Only a finite number of clock domains are supported on any given FPGA!

Miscellaneous “low speed” logic, e.g., a serial DAC or thermometer, doesn’t need a separate clock domain! If the logic is clean, it will make timing at the primary clock rate. Simply put clock-enables on all its registers to slow down its sequencing.

- Saves the clock domains for essential uses
- Simplifies attachment to the rest of the chip’s logic.

Metastability

 


- A metastable state is one in which the output of Flip-Flop is unknown,
- When setup or hold time are violated.
- Input data must be stable within t_s and t_h .
- Signal propagation time must be analyzed to avoid metastability
- Most conditions occur in:
 - Sampling a signal external to the FPGA (such as ADC, clock);
 - Crossing clock domains;

Crossing clock domains

Multi-cycle signal

 problem Metastability

solution Pipeline twice in receiver domain.



Single cycle flag

problem Missing flag, metastability

solution Convert flag to toggle, latch twice

Data bus (≥ 2 bits)

problem misaligned bits

solution1 Gray code

solution2 First-In-First-Out (FIFO) buffer

On-chip memory


- Small, granular, flexible, fast:
 - Xilinx: 16 to 64 bits each, one-bit access
 - Altera: 32x20 or 64x10 in some chip families
- Block memory: dual-port, 4K to 36K bits each, 1 to 36 bit data ports
- Large block: single-port (rare)

On-chip memory: just inferred from HDL

Off-chip memory: slow, more difficult to use and simulate

Putting things together

Design Process:

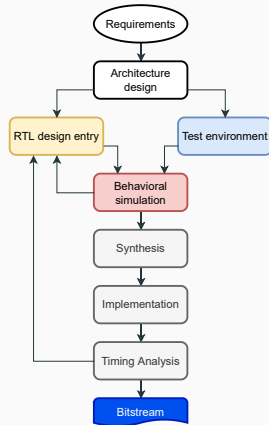

- Hardware Description Language (HDL):
 - VHDL, Verilog, SystemVerilog
- Simulation tools:
 - Icarus Verilog
 - Verilator
 - Mentor Graphics ModelSim, Xilinx Vivado Simulator, etc.
- Synthesis tools:
 - AMD Xilinx Vivado
 - Intel Quartus
 - Yosys Open Synthesis Suite

Check your design (timing, utilization, power) reports!

LLRF system architecture: System-On-Chip

